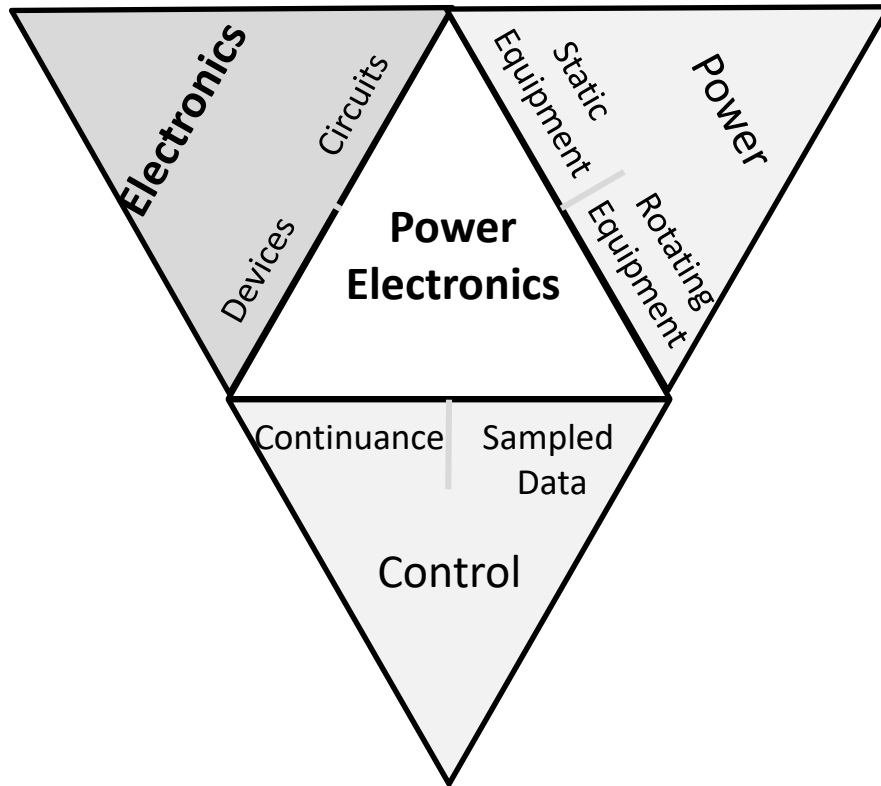


SIMetrix/SIMPLIS Simulation for Power Electronics


Contents

- 1. PE(Power Electronics) and Simulation**
- 2. SIMetrix/SIMPLIS 특징**
- 3. Components SPICE/PWL Model**
- 4. PE Example**

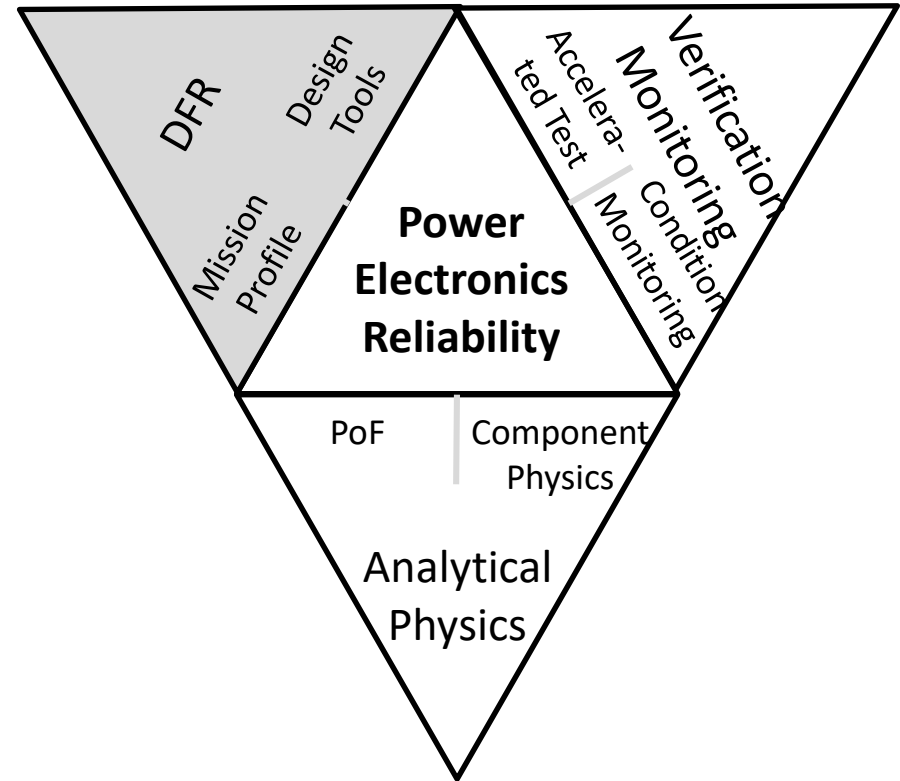1-1 Scope of Power Electronics and Reliability




**Power Electronics
by William E. Newell in 1970**




**Power Electronics Reliability
by CORPE in 2010**

The center addresses a better understanding of how the reliability of power electronic devices and systems is influenced by different stress factors such as **temperature**, **overvoltage** and **current**, and **overload** and **environment**.

1-2 High Quality PE Design Flow

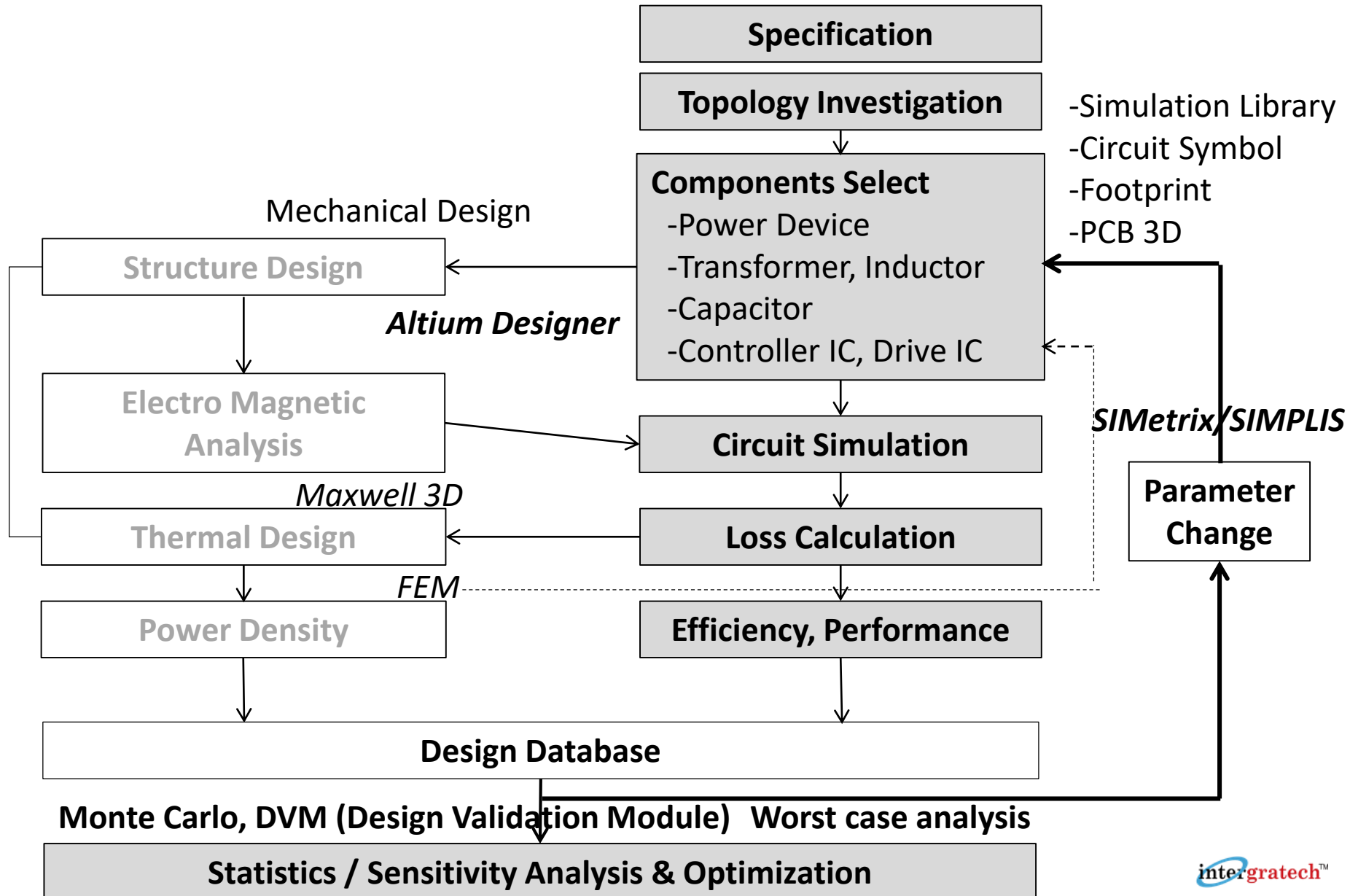


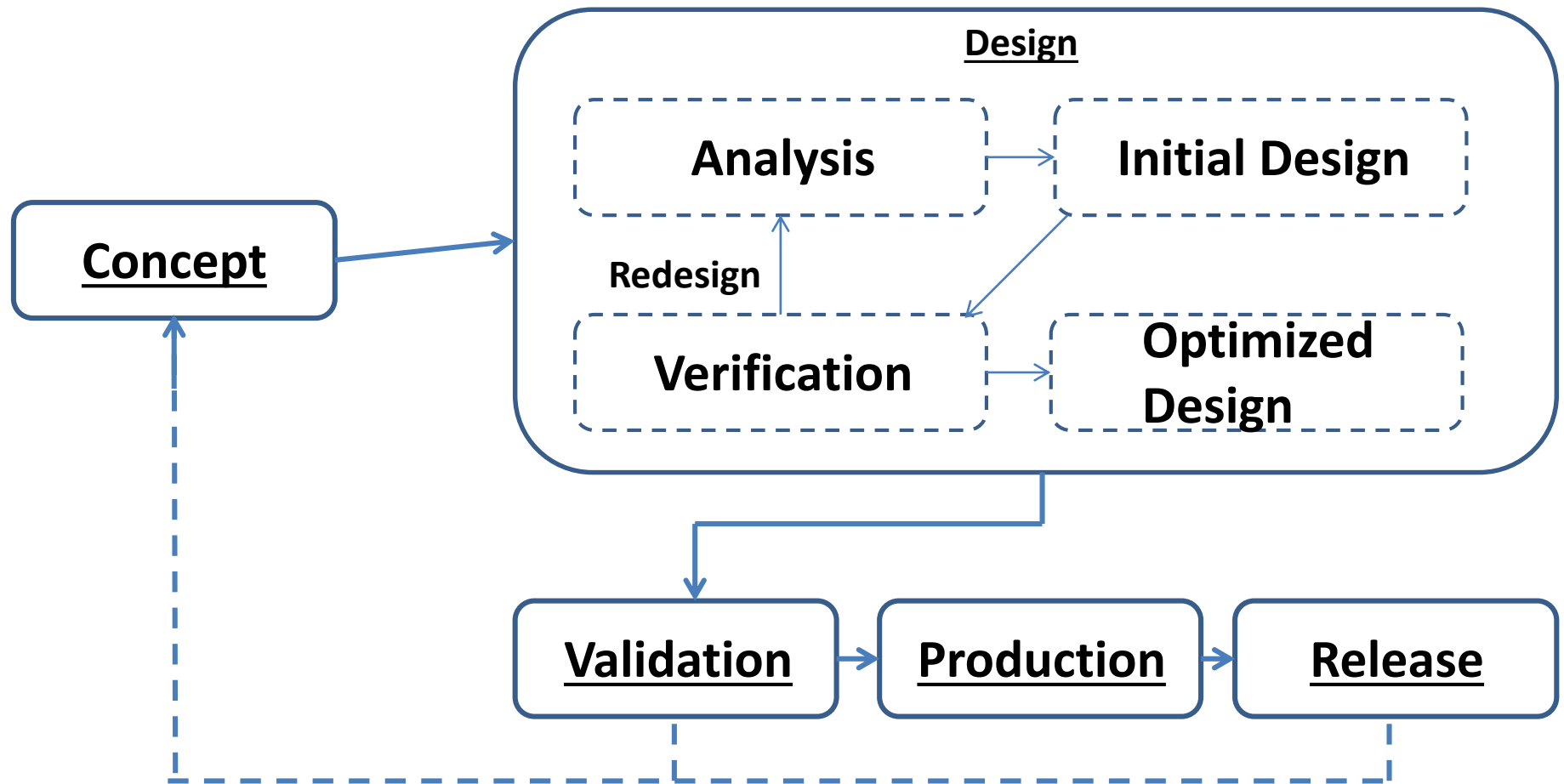1-3 State of Reliability Design Procedure for Power Electronics Systems



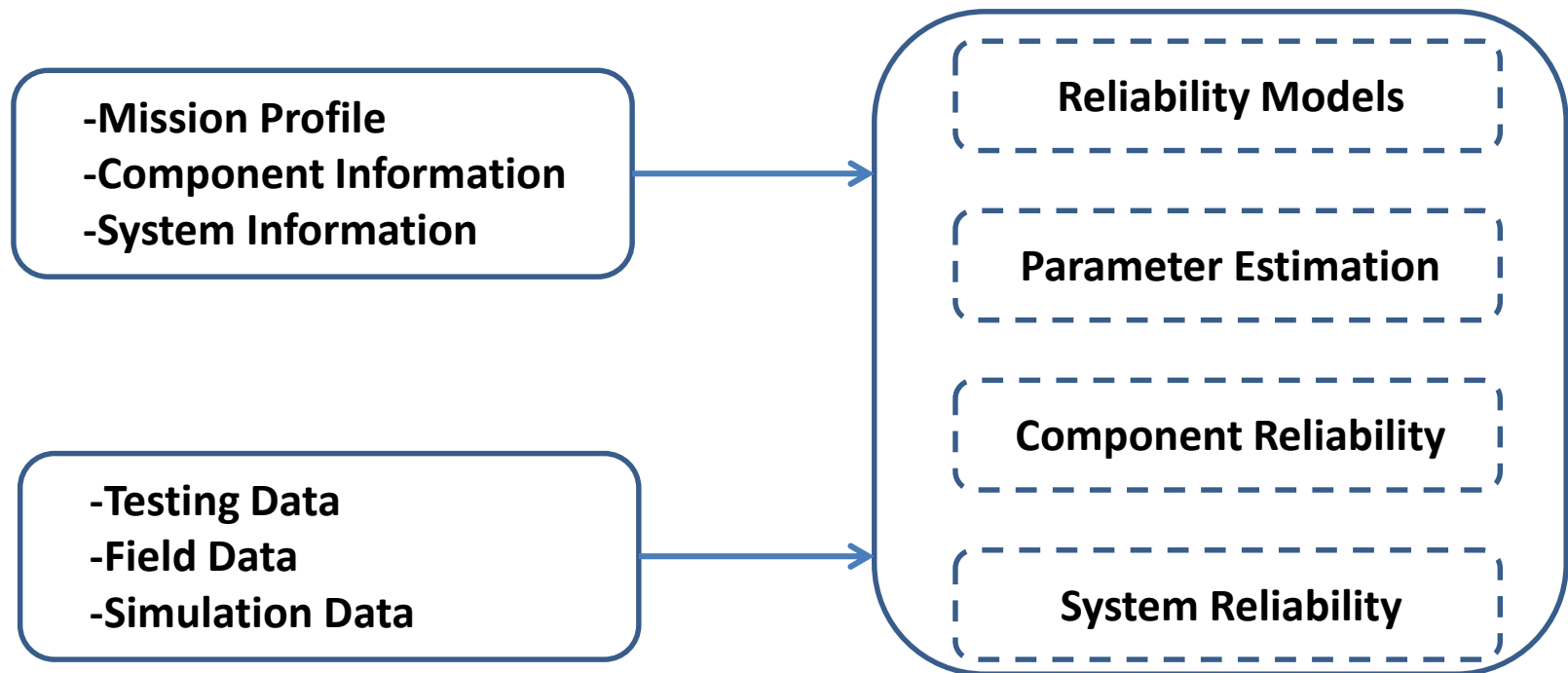1-4 High Quality Design Methods

- Safety factors / derating, -worst-case analysis
- Six sigma design, -Statistical design of experiments
- Taguchi design approach
design approach tests the effect of variability of both control factors and noise factors



Contents

1. PE(Power Electronics) and Simulation
- 2. SIMetrix/SIMPLIS 특징**
3. Components SPICE/PWL Model
4. PE Example

2-1 PE회로 해석에 적용한 Simulator 종류

Simulator	EMTP	SPICE	SABER	SIMPLIS	SCAT	KREAN	PSIM	SIMPROLA	MATLAB/ SIMILINK
수치적분법	Trapezoidal	Trapezoidal (Default), Gear	Gear (Default), Trapezoidal	선이행열 급수전개 근사법	Trapezoidal	Semi-implicit Runge-Kutta	Trapezoidal	-	Runge-Kutta (Default)
회로 정식화	절점해석	수정절점해 석	수정접점해 석	상태변수해 석	상태변수해 석	상태변수해 석	절점해석	절점해석	상태변수해 석
계산Step	Fix(지정)	Variable (자동)	Variable (자동)	Variable (자동)	Variable (자동)	Variable (자동)	Fix(자동)	Variable	Fix/Variable 선택 가
계산Step	Ideal switch	Ideal / Non lineal / 소자 모델링	Ideal / Non li neal / 소자 모델링	Ideal / Non li neal / 소자 모델링	Ideal	Ideal	Ideal	Ideal	Ideal
Switch시의 취급	영점보상 없음	오차평가가 수속할때까 지 Step을 재계산	전후값으로 보간	전후값으로 보간	Newton법과 2분법	전후값으로 보간	영점보상 없음	-	없음
개발목적	계통Surge 해석	집적회로 설계	시스템 설계	Switching 전원설계	Switching 전원설계	PE회로	PE회로	PE회로	제어계 설계
분야	회전기 /계통 해석	소자모델 포함 상세한 해석	기계/열계 등과 연동 해석	同上	同上	Motor제어	同上	Magnetics/F EA 해석과 연동 가능	同上
그외	-	User가 많고 교육용서적 풍부	MAST언어 로 모델구축가 능 SPICE호완 Lib 있음	주기정상상 태 / 주파수해석 이 가능	주기정상상 태/주파수 해석이 가능	-	PE model LIB있음	ANSIS가 제공하는 Simulator module로 시스템 구축 용이	Power System Blockset 로 support

2-2 Switching Mode PE향 Simulator

-Switching 회로를 고속으로 Simulation 가

-SIMPLIS

-1989 Duke대학교에서 AT&T향으로 개발. 현재는 Transim
SPICE계SIMetrix와 통합한 SIMetrix/SIMPLIS
SIMPLIS->System Level를 고속으로, SIMetrix->고정도
Switching회로를 포함한 System의 AC 해석이 가능

-SCAT

-1992 Shojo대학교 Nakahara교수 개발
-Switching전원 해석/설계용

-PSIM

-1995 British Columbia대학교(Canada)에서 개발
-PE용. 전자계Soft JMAG와 연성가능

-System의 Hybrid성, -System의 Nonlinear성

-Switching의 문제, -Stiff

<http://www.simplistechnologies.com/>



SIMPLIS
TECHNOLOGIES

Site Map
▼ SIMetrix/SIMPLIS

SIMetrix / **SIMPLIS**

» *CIRCUIT SIMULATION SOFTWARE FOR POWER ELECTRONICS DESIGNERS*

<http://www.simetrix.co.uk/site/index.html>



Versatile Circuit Simulation

User support
+44 (0)1635 866395

[Home](#) [Products](#) [License options](#) [Why choose SIMetrix](#) [Support](#) [About us](#) [Contact us](#)

Used by the world's leading
electronics companies

<http://www.igtech.co.kr/>



아이디 비밀번호 비밀번호 기억 회원등록 | 비밀번호찾기 English 사이트맵 Contact us

[회사소개](#) [제품소개](#) [자료실](#) [Q&A](#) [동영상](#) [커뮤니티](#)

[Altium Designer](#) [Yenka](#) [CAM350](#) [PCB 샘플제작라인](#) [AutoVue](#) [SIMPLIS](#)

제품소개

[Altium Designer](#)
[Yenka](#)
[CAM350](#)
[PCB 샘플제작라인](#)
[AutoVue](#)
[SIMPLIS](#)



SIMetrix / SIMPLIS

심플리스 SIMPLIS

Home > 제품소개 > 심플리스



Simulation Software for Power Electronics

SIMetrix / **SIMPLIS**

[TOP](#)

When SIMPLIS? When Spice?

- Spice is optimized for:
 - Circuits that can be linearized around a DC operating point
 - e.g. Op amp circuits, ...
 - IC circuits where Spice models can relate device parameters to process parameters
- SIMPLIS is optimized for switching systems that have:
 - Very fast switching transients and relatively large amounts of energy storage
 - e.g. Closed-loop switching power supplies, Switched capacitor filters, Phase-Locked Loops

SIMPLIS makes Virtual Prototyping Feasible

- For closed-loop switching power supplies,
 - **Vastly superior speed** for transient simulations
 - Typically 10X to 50X faster than Spice
 - **Vastly superior convergence** properties
 - Convergence ceases to be an ever-present concern
 - Ability to quickly find **steady-state** and do **AC analysis** for circuits that have a stable steady-state limit cycle using only the large signal time-domain model – ***no derivation of an average model required***

... make Virtual Prototyping Feasible

2-3 SIMetrix/SIMPLIS 기능

SIMPLIS 의 Simulator 기능

- Transient Analysis (TX) : Transient Waveform
- Periodic Operating Point (POP) : Stead State Waveform
- Frequency Analysis (FX) : Bode Diagram

-SIMetrix의 Simulator 기능

- Transient, -AC Analysis, -DC Sweep, -Noise Analysis
- Transfer function, -Monte Carlo Analysis, -Pole-zero Analysis

-Verilog Co-Simulation

- Analog Circuit와 Verilog-A 및 Verilog-HDL의 Co-Simulation 지원

-Script Edit

-DVM(Design Validation Module)

-SystemDesigner(Support Piccolo)

2-4 PE에 대한 Simulator측의 대책

- Switching 회로 문제의 대책
 - Switching Device Model 의 Level선택(1,2,3)
 - 엄밀한 Dynamic Model -> 상태평균화Model
 - 회로정식화범의 선택
 - SPICE : 수정절점해석
 - SIMPLIS : 상태변수해석
- 수치적분법의 적정화
 - Tapezoidal
 - Gear-2
- 계산알고리즘 개량

About Transim

News & Events

2014-2-4 MOSFET Selection was never so easy with Toshiba's Web Simulator

2014-1-6 Jumpstart Board Design with GE's Power Module Wizard

2013-11-7 Fairchild's Power Supply WebDesigner Enhanced with Power Train Discrete Device Power Loss and Efficiency Analysis Tools

Transim Technology Corporation is the global leader in delivering innovative cloud application engineering solutions for online design support in the electronics industry.

[Learn More>>](#)

Who's using Transim?



ON Semiconductor






Contents

1. PE(Power Electronics) and Simulation
2. SIMetrix/SIMPLIS 특징
- 3. Components SPICE/PWL Model**
4. PE Example

3-1 Main Components of Power Electronics

Item		Parameters
Switching Device	Ideal Device	$R_{on}=0, R_{off}=\infty, V_{on}=0, T_{sw}=0, C_{par}=0, L_{par}=0$
	Diode	$V_f=0.3V \sim 2V$
	MOSFET	$1m\Omega \sim 10\Omega, V_{ds}=10V \sim 1500V$
	IGBT	$V_{on}=1.3V \sim 3V, V_{ces}=200V \sim 1700V$
Energy Storage Device	Inductor L	$1/2LI^2$
	Capacitor C	$1/2CV^2$
Lose Device	Resistance R	RI^2
Control Device	IC	Amp, Drive, DSP, FPGA, ASIC...

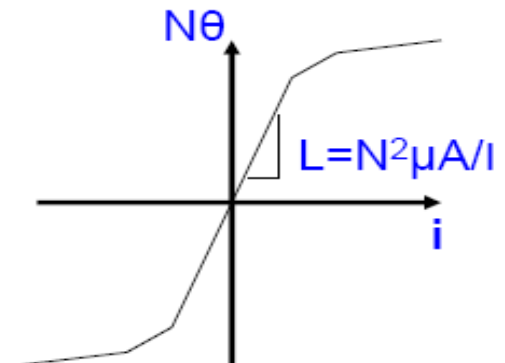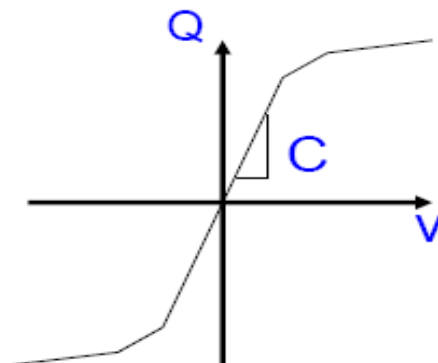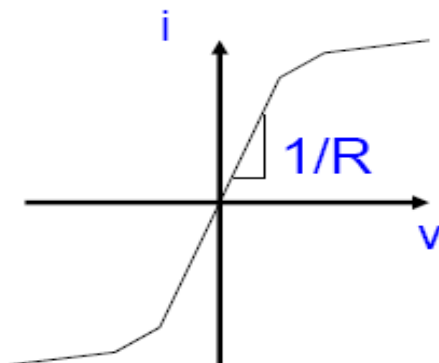

Piecewise Linear Components (SIMPLIS)

3-2. Device Model

-Device Model(SPICE Model)

전자부품(반도체부품, 수동부품등)의 전기적 거동 표현

-SIMetrix의 Device Model는 SPICE기술.

-SIMetrix/SIMPLIS 의 Components는 크게 두가지

-Genric Components

RCL, DC/AC Source, ADC, DAC, Digital Generic등

-수식모델

Non-liner Transfer Function, Laplace Transfer Function

Multi Level Modeling(SIMPLIS)

Level 1 : Ideal


Level 2 : Stability Analysis

Level 3 : High di/dt Load Transient

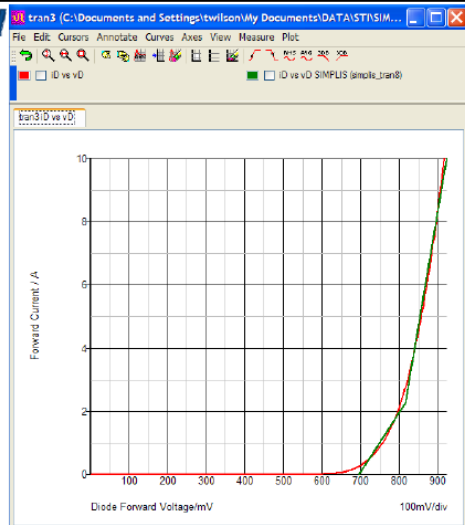3-3. Device Model


Diode PWL Model

- Three-segment SIMPLIS diode model (green)
- Compared to Spice model (red)
- Fit optimized over 4A – 8A range




FET PWL Model

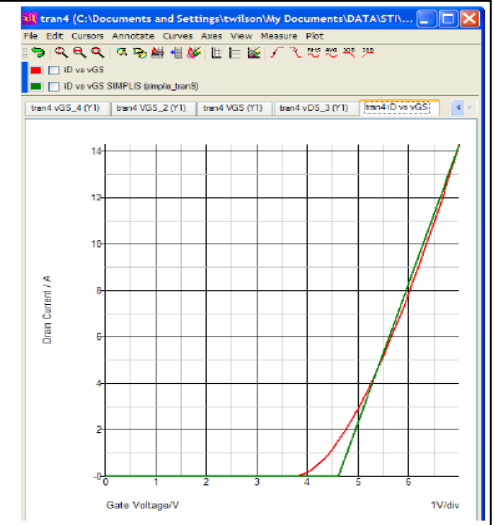
- Two-segment SIMPLIS I_D vs. V_{GS} (green)
- Compared to Spice model (red)
- Fit optimized over 33% - 100% of I_{max}




N –Channel MOSFET SIMPLIS Model

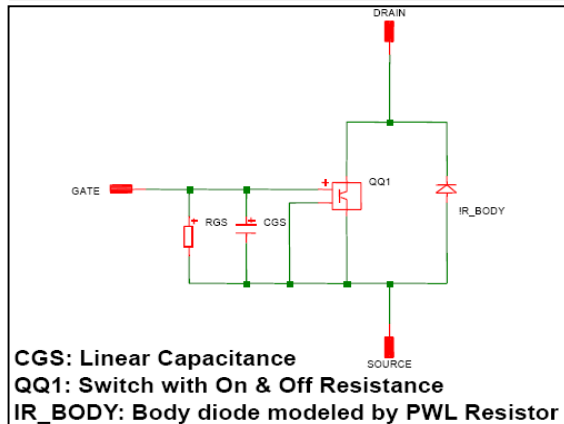

Level 1

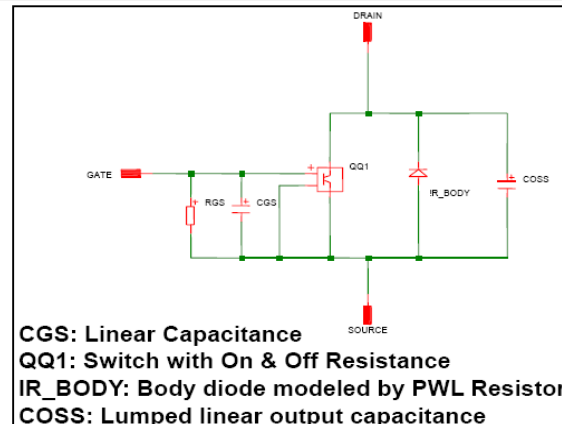

Level 2

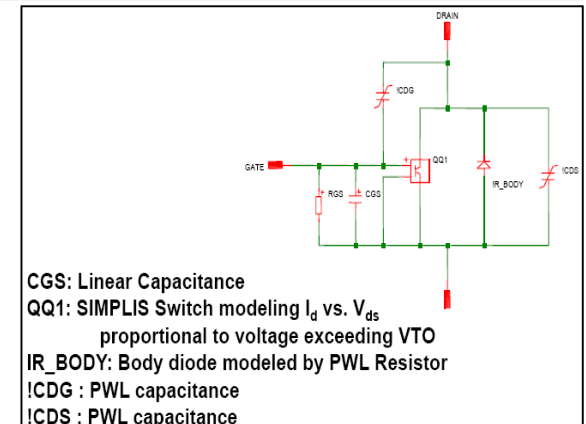

Level 3

Model Accuracy

- **Accuracy of Physics:** the Physics behind the equations that describe semiconductors
 - Spice - very accurate
 - SIMPLIS – piecewise linear behavioral approximations
- **Accuracy of Parameters:** the value of the constants used in the model
 - Spice – mere mortals cannot typically create their own Spice models
 - SIMPLIS – models are based on data sheet info and can be created by average user in ~20 minutes
- **Accuracy of solution of circuit equations:**
 - Spice – in order to get practical speed, Spice must accept more numerical error (RelTol) per computational step
 - SIMPLIS – takes advantage of piecewise linear system to get extremely accurate numerical solutions of circuit equations

SIMPLIS

- Because SIMPLIS can get extremely accurate numerical solutions to the circuit equations:
 - SIMPLIS can solve numerically for the steady-state limit cycle of a closed-loop switching power supply very quickly
 - % change in all state variables from beginning to end of one conversion cycle $< 10^{-10}$ %
 - SIMPLIS can perform a small signal analysis on the full large signal model of the power supply (no need to derive a separate averaged model)

Contents

1. PE(Power Electronics) and Simulation

2. SIMetrix/SIMPLIS 특징

3. Components SPICE/PWL Model

4. PE Example

- Non Insulation type

 - Buck type DC-DC Converter

 - Boost type DC-DC Converter

 - Boost type AC-DC Converter

- Insulation type


 - Flyback DC-DC Converter

 - Full Bridge DC-DC Converter


- Single Phase DC-AC Inverter

4-1. Buck DC/DC Converter Design

Base on the SIMetrix/SIMPLIS Simulator

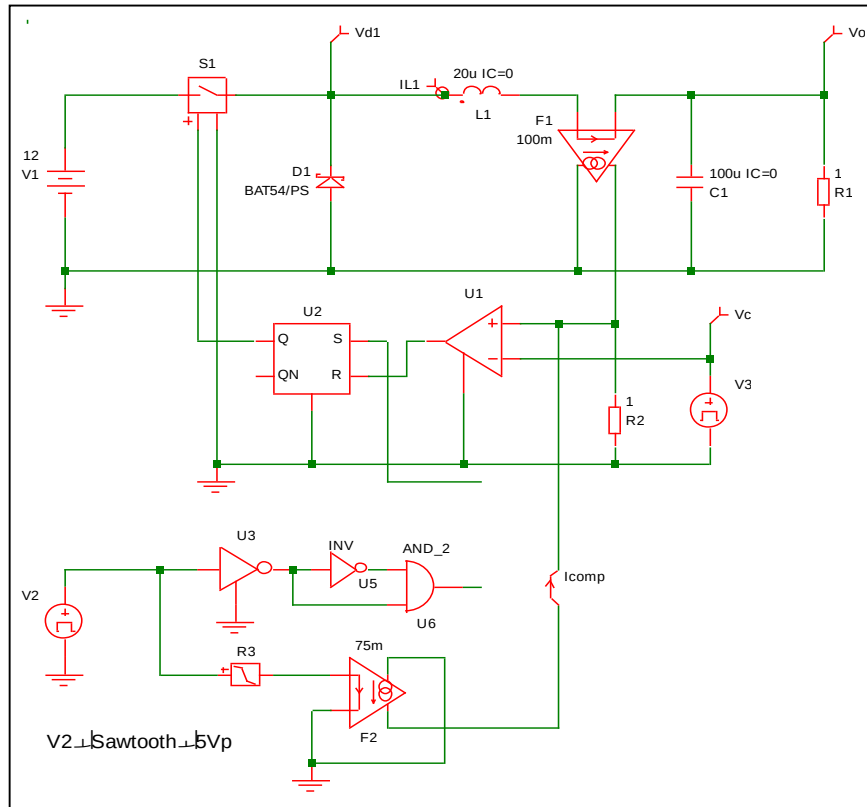


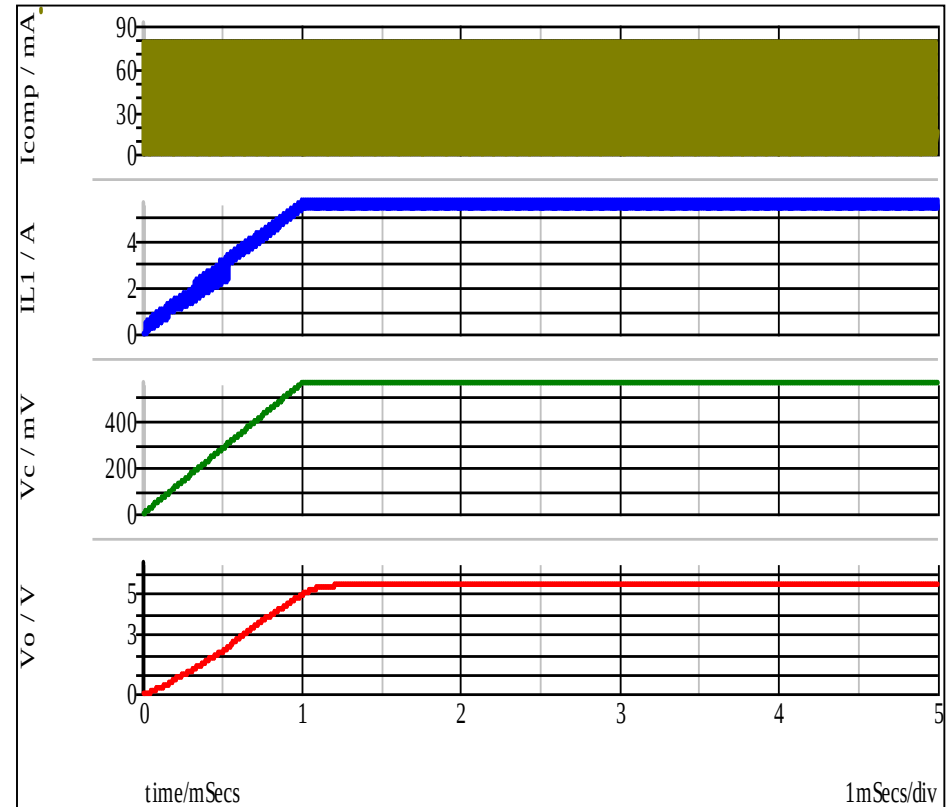**Current Mode Control
Buck DC-DC Converter**




Start Response

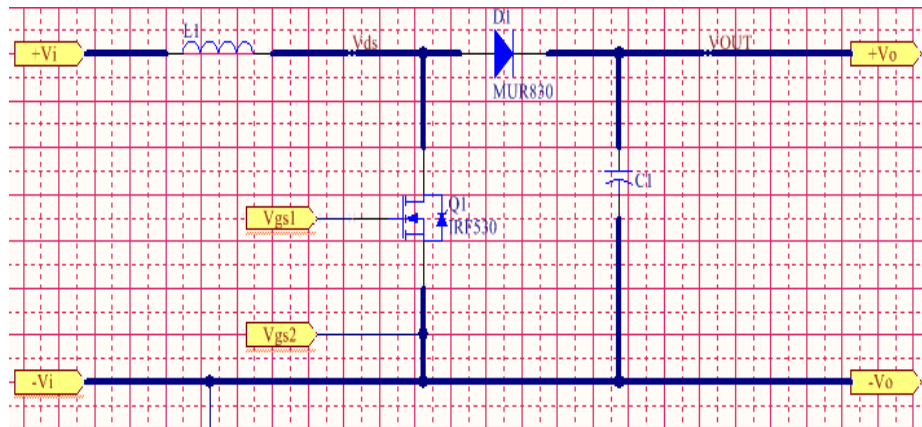
4-2 Base on the Altium Designer Using SIMPLIS Simulator



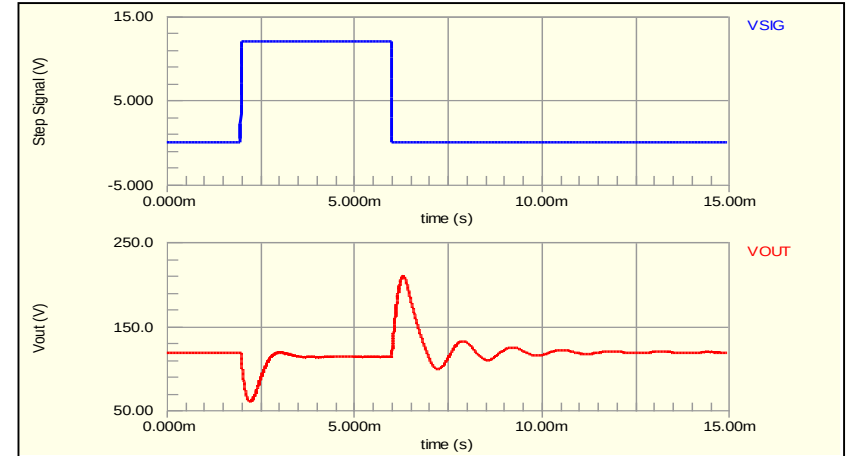**Boost DC-DC Converter Design
Base on the Altium Schematic**




Step Response

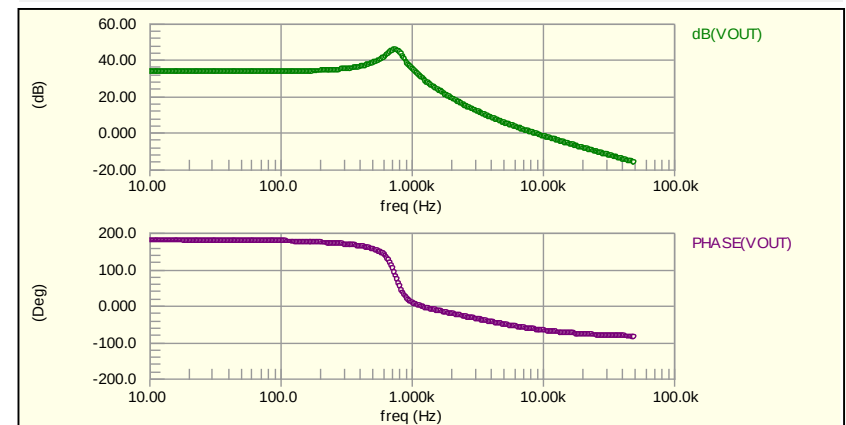


Frequency Response

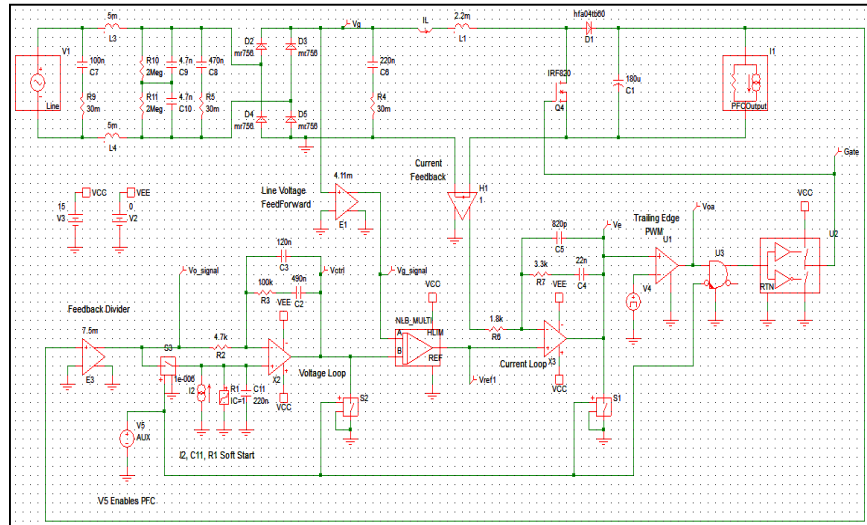4-3 Single Phase AC-DC Converter(SIMetrix) -Average Current Control Method




Single Phase AC-DC Converter

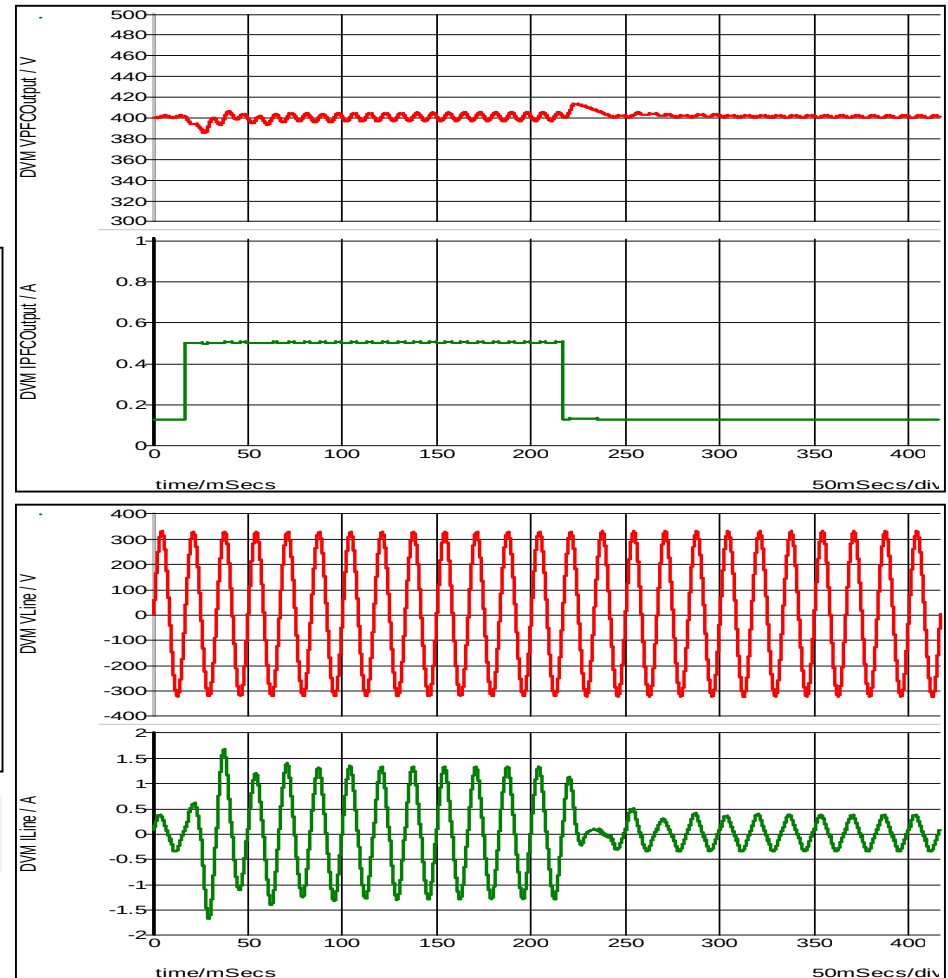


Load Step Response

4-4 Flyback DC/DC Conv.


Design Base on the Altium Schematic

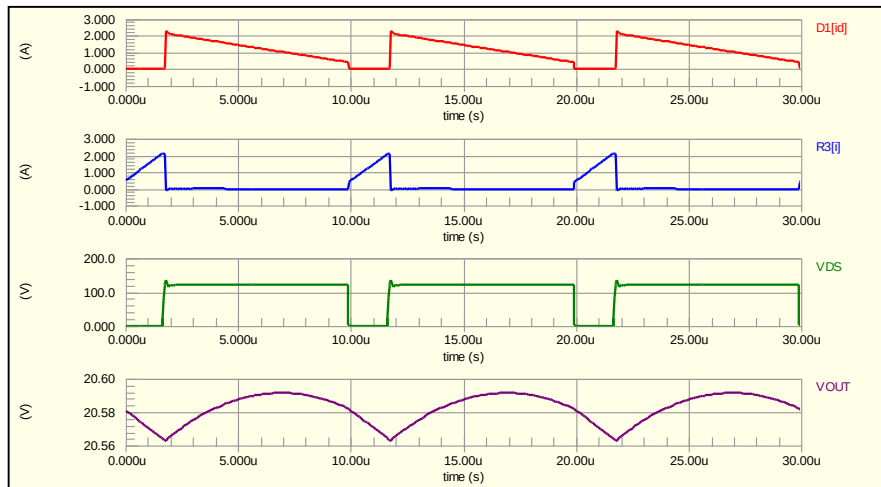


Switching Waveform (DCM)

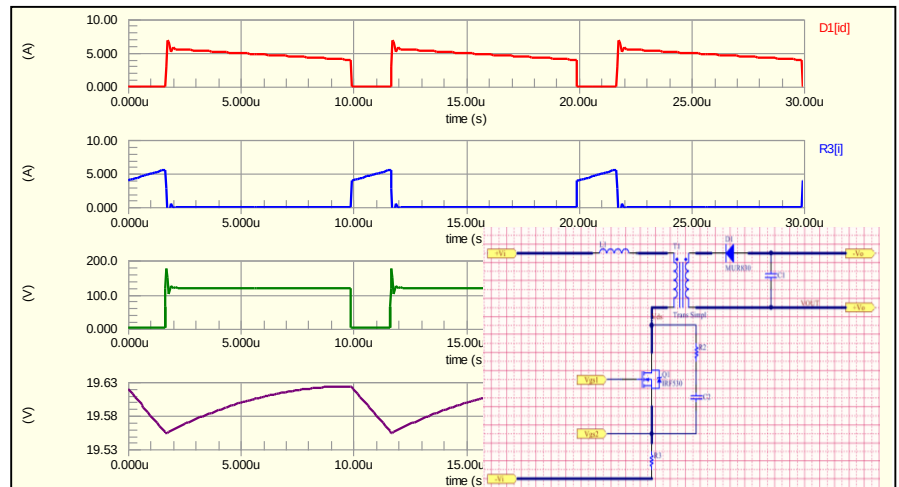

Switching Waveform (CCM)

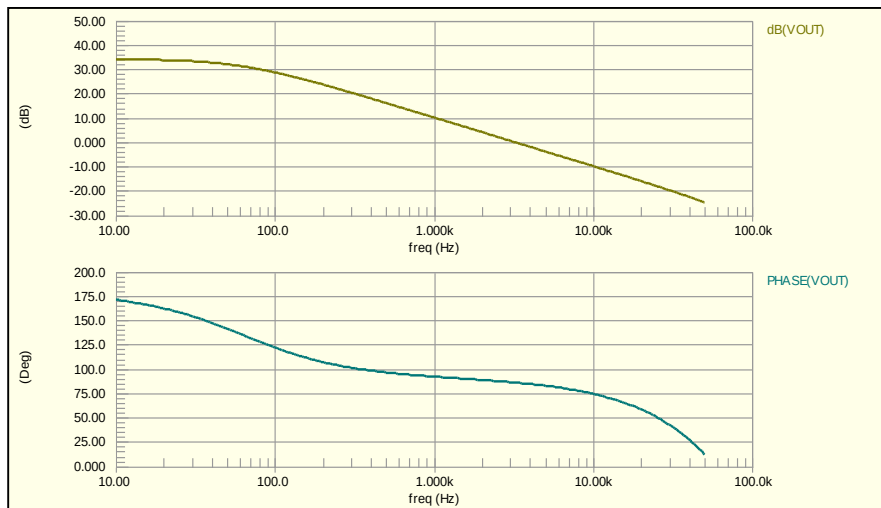


Frequency Response (DCM)

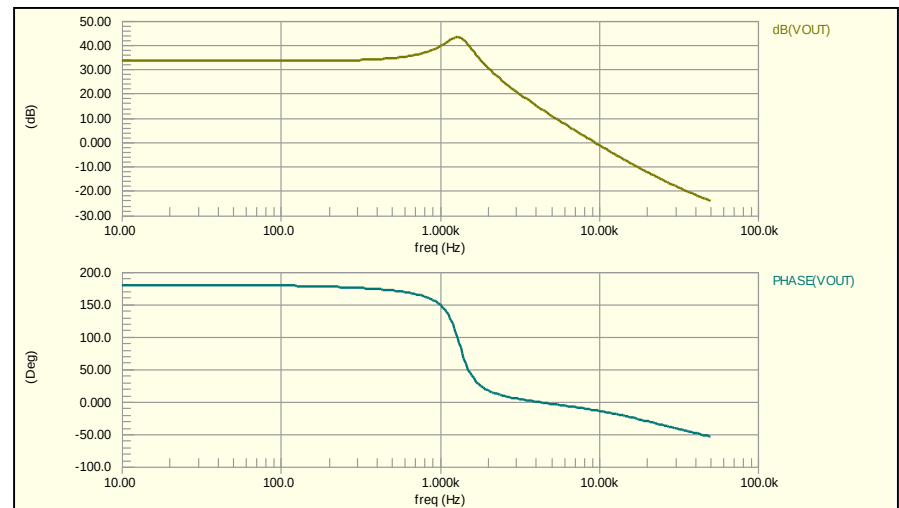


Frequency Response (CCM)

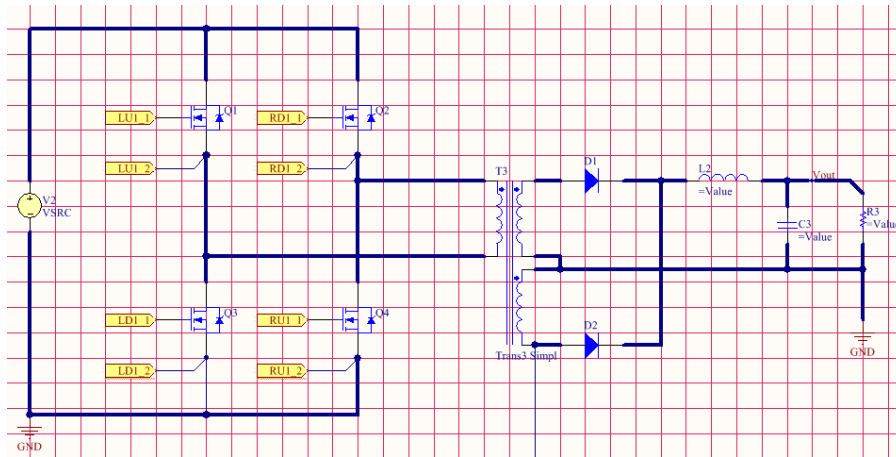
4-5.Base on the Altium Designer Using SIMPLIS Simulator(1/2)



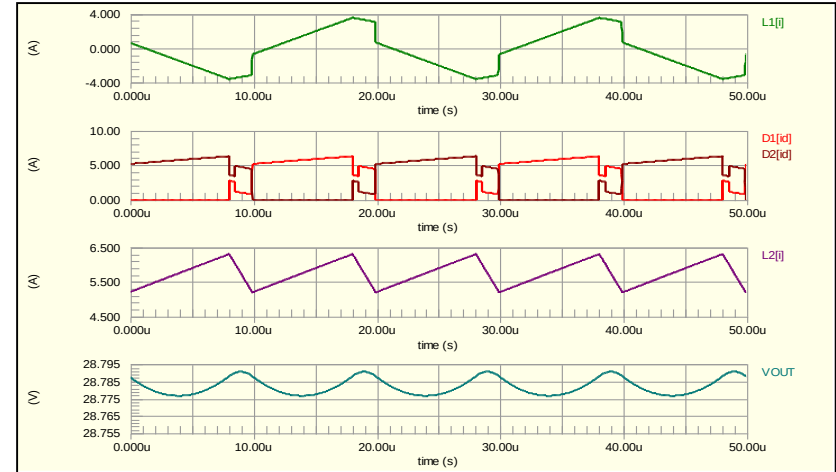**Phase Shift Full Bridge
DC-DC Converter Design
Base on the Altium Schematic**



Switching Waveform

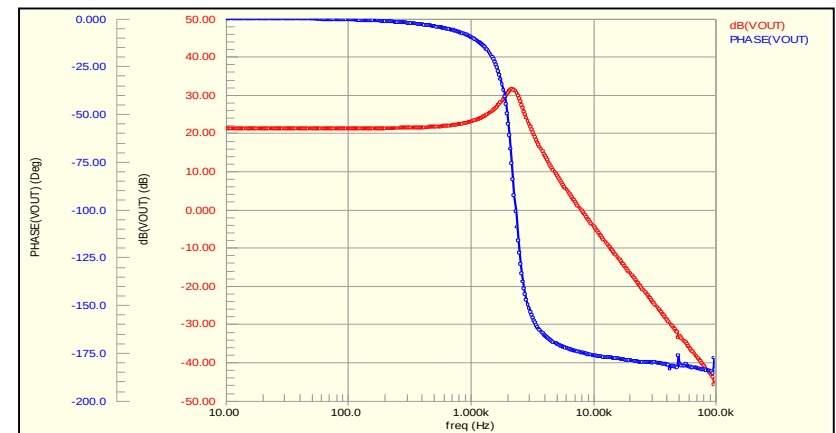

Frequency Response

4-5. Base on the Altium Designer Using SIMPLIS Simulator (2/2)

Bill of Materials For PCB Document [Full-Bridge Converter pcbDoc]

Comment	Description	Designator	Footprint	LibRef	Quantity
Cap	Capacitor	C2, C3, C4, C5, C6, C7, C8	Cap	Cap	7
Cap2	Capacitor	C9, C10	CAP15-4x5	Cap2	2
MUR830	General Purpose Fast Rec	D1, D2	TO-220AB	Diode MUR830	2
Diode 1N4148	High Conductance Fast R	D3, D4, D5, D6, D7, D8	DO-35	Diode 1N4148	8
IPWL	Piecewise Linear Current	I1	HDR15-2CH	IPWL	1
Inductor	Inductor	L2	0402-A	Inductor	1
Inductor Iron Dot	Magnetic Core Inductor w. Lout		DIODE_SMC	Inductor Iron Dot	1
IRF840	HEFET N-Channel Pow	Q1, Q2, Q3, Q4	TO-220AB	IRF840	4
2N2906	PNP General Purpose Am	Q5, Q6, Q7, Q8	TO-92A	2N2906	4
Res1	Resistor	R1, R2, R3, R4, R5, R6	A2GAL-0.3	Res1	16
Trans3 Ideal	Three-winding Transformer	TX1	TRF_5	Trans3 Ideal	1
Trans Ideal	Transformer (Ideal)	TX2	TRF_4	Trans Ideal	1
Trans5 Ideal	Five-winding Transformer	TX3	TRF_10	Trans5 Ideal	1
Designator UC3905	UC3905 PSIU Controller	U1	DIP-16	UC3905	1
Designator V1	Piecewise Linear Voltage	V1, V4	HDR15-2CH	VPWL	2
Designator VSIN	Sinusoidal Voltage Source	V3	HDR15-2CH	VSIN	1

Export Options: File Format: Microsoft Excel Worksheet [xls, xlsx, xlt, xlsx] Add to Project Open Exported

Supplier Options: (none) Production Quantity: 1 Round up Supplier Order Qty to cheapest price break Use cached pricing data in parameters & offline

BOM

Add Supplier Links


Keywords: IRF840

Manufacturer	Manufacturer Part Number	Supplier	Description	Unit Price
VISHAY SILICONIX	IRF840ASPB	Newark	VISHAY SILICONIX IRF840ASPB, N-CHANNEL MOSFET, 500V, 8A, D2-PAK	1.59 USD
Vishay Siliconix	IRF840ASTRLPBF	Digi-Key	MOSFET N-CH 500V 8A D2PAK	226 KRW
Vishay Siliconix	IRF840ASTRLPBF	Digi-Key	MOSFET N-CH 500V 8A D2PAK	226 KRW
Vishay Siliconix	IRF840ASTRLPBF	Digi-Key	MOSFET N-CH 500V 8A D2PAK	226 KRW
VISHAY SILICONIX	IRF840ASTRLPBF	Newark	VISHAY SILICONIX IRF840ASTRLPBF, MOSFET, N-CH, 500V, 8A, TO-263-3	1.59 USD
Vishay Siliconix	IRF840LCPBF	Digi-Key	MOSFET N-CH 500V 8A TO-220AB	1808 KRW
VISHAY SILICONIX	IRF840LCPBF	Farnell	VISHAY SILICONIX IRF840LCPBF, N-CHANNEL MOSFET, 500V, 8A TO-220AB	1.908 GBP
VISHAY SILICONIX	IRF840LCPBF	Newark	VISHAY SILICONIX IRF840LCPBF, N-CHANNEL MOSFET, 500V, 8A TO-220AB	1.59 USD
Vishay	IRF840PBF	Digi-Key	MOSFET N-CH 500V 8A TO-220AB	1796 KRW

Results 1 to 37 of 76 (2 errors)

Name: IRF840LCPBF
Category: MOSFET
Description: MOSFET N-CH 500V 8A TO-220AB
FET 유형: MOSFET N-Channel, 금속 산화물
FET 특징: 표준
Id 기준 Vgs(th) (최대): 4V @ 250uA
Manufacturer: Vishay Siliconix
Manufacturer Part Number: IRF840LCPBF
Rds On (최대) @ Id, Vgs: 850m @ 4.8A, 10V
RoHS Compliant: Yes
Supplier: Digi-Key
Supplier Part Number: IRF840LCPBF-ND
게이트 전압(Vgs) @ Vds: 39V @ 10V
평균 방열 패키지: TO-220AB
드레인 - 소스 전압(Vds): 500V
실장 유형: 스프롤

Supplier Link

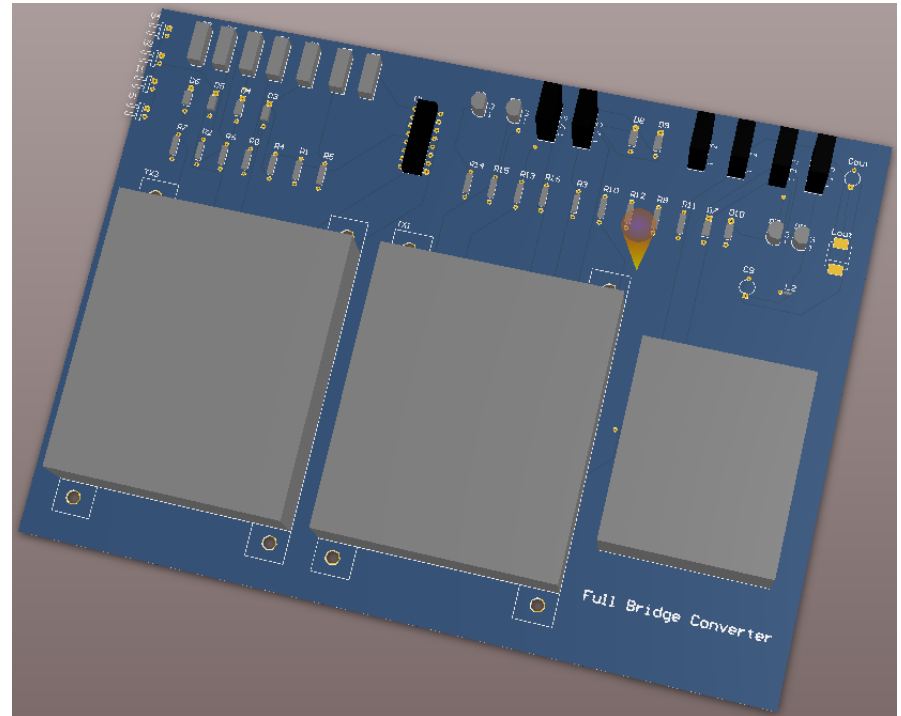


PCB

The figure displays the frequency response and internal structure of a two-stage operational amplifier. The top plot shows the Gain in dB versus Frequency in Hertz, with the gain peaking at approximately 0 dB around 50 Hz. The bottom plot shows the Phase in degrees versus Frequency in Hertz, with the phase shifting from approximately 60 degrees at 20 Hz to -20 degrees at 200 Hz. The block diagram illustrates the internal components, including two input stages (N1, N2) and two output stages (N3, N4), connected in a two-stage configuration. The input signal is applied to the non-inverting input (N1) and the output is taken from the inverting input (N2). The output stages (N3, N4) are connected to the output nodes (OUT, IN) and provide a gain of 33.4 (approximately 30 dB).


The figure displays four stacked oscilloscope waveforms over a 200 ms time interval. The top trace (purple) shows the input current I_{in} in Amperes (A), which is a high-frequency sinusoidal wave oscillating between approximately -10 A and 10 A. The second trace (yellow) shows the phase in Volts (V), which is a high-frequency sawtooth wave oscillating between -2 V and 2 V. The third trace (blue and green) shows the voltage V in Volts (V), with two sinusoidal waveforms oscillating between -10 V and 10 V. The bottom trace (red) shows the output voltage V_{out} in Volts (V), which is a sinusoidal wave oscillating between -400 V and 400 V. A vertical blue line at 100 ms is labeled "Grid connect", indicating the point of connection to the grid.



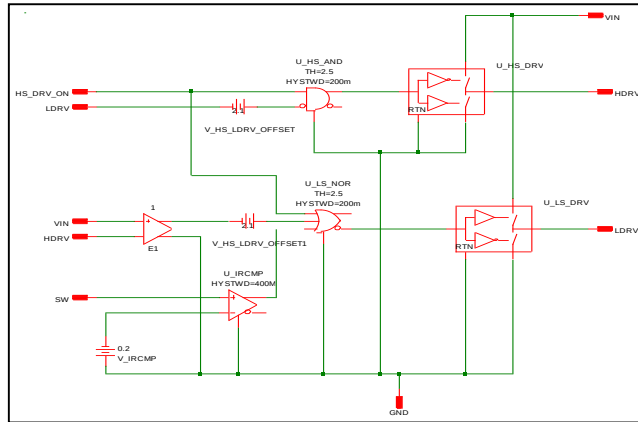
4-7. Control IC Design & Hierarchy Structure




Drive Circuit

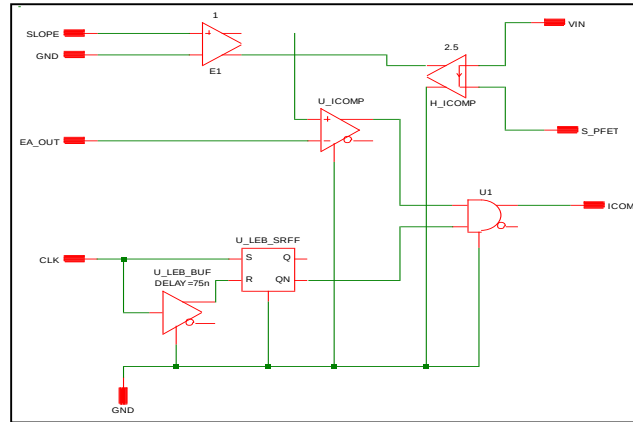

Switching Logic

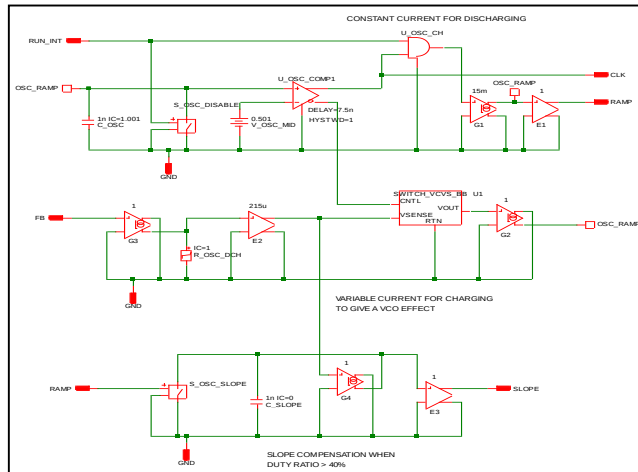


Function / Feedback Block

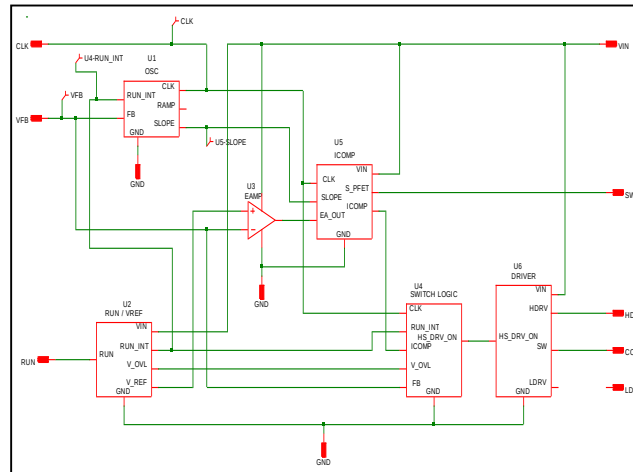


Control IC

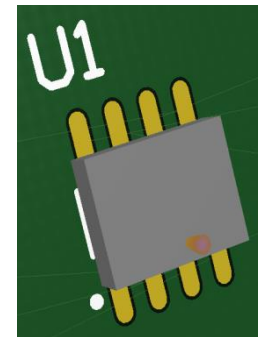- Simulation Library
- Circuit Symbol
- Footprint
- PCB 3D




Footprint & PCB 3D


4-8. Monte-Carlo Analysis

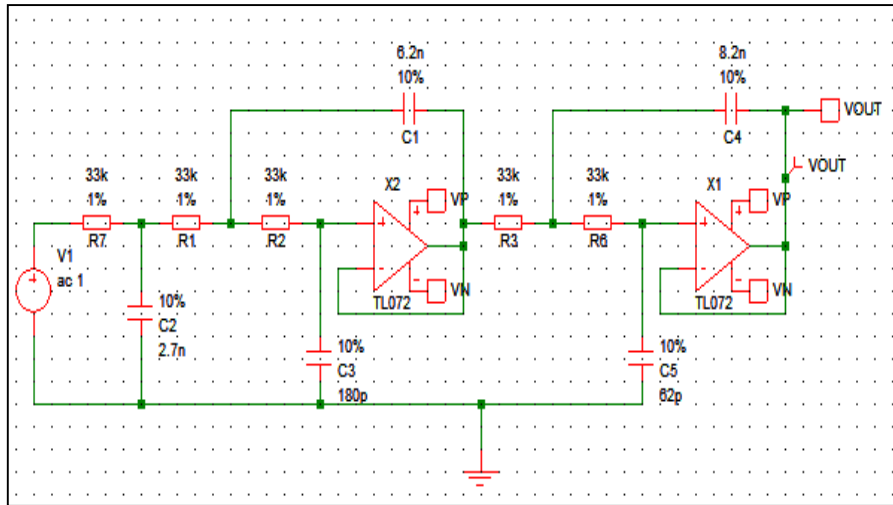

Active filter

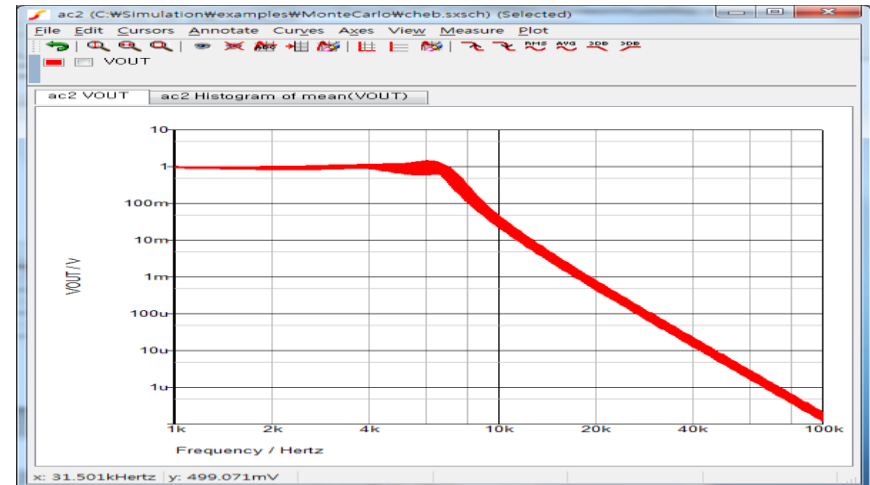

Response Result

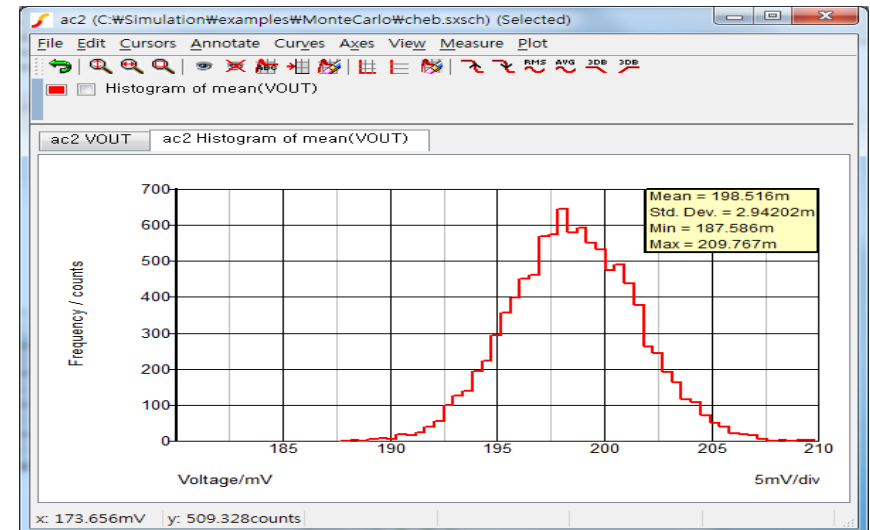

Histogram

4-9. DVM(Design Verification Module)(1/2)

-AC Analysis

**Bode Plot, Conducted Susceptibility, Input Impedance,
Output Impedance**

-Transient Analysis

Step Load, Step Line, Startup, Short Circuit

-DC-DC, AC-DC Steady-State Analysis

POP(Periodic Operating Point)(Only DC-DC),

Line and Load Regulation, Efficiency, Power loss

AC Analysis(Only DC-DC), Input/Output Impedance

-Sensitivity / Worst Case Analysis


-Audit Circuit for Worst Case, Definition

4-9. DVM(Design Verification Module)(2/2)

dvm_advanced.testplan - 개요창

analysis	objective	source	load	label	Measurement	Measurement	Measurement	Measurement
Steady-State	Steady-State	"SOURCE (INPUT-1, Nominal)"	"LOAD (OUTPUT-1, Light)"	Steady-State	Steady-State	Vin Nominal	Light Load	*Alias Efficiency_Efficiency_nom
Steady-State	Steady-State	"SOURCE (INPUT-1, Nominal)"	"LOAD (OUTPUT-1, 100%)"	Steady-State	Steady-State	Vin Nominal	100%	*Alias Efficiency_Efficiency_nom
Steady-State	Steady-State	"SOURCE (INPUT-1, Nominal)"	"LOAD (OUTPUT-1, 20%)"	Steady-State	Steady-State	Vin Nominal	20%	*Alias Efficiency_Efficiency_nom
Steady-State	Steady-State	"SOURCE (INPUT-1, Nominal)"	"LOAD (OUTPUT-1, 30%)"	Steady-State	Steady-State	Vin Nominal	30%	*Alias Efficiency_Efficiency_nom
Steady-State	Steady-State	"SOURCE (INPUT-1, Nominal)"	"LOAD (OUTPUT-1, 40%)"	Steady-State	Steady-State	Vin Nominal	40%	*Alias Efficiency_Efficiency_nom
Steady-State	Steady-State	"SOURCE (INPUT-1, Nominal)"	"LOAD (OUTPUT-1, 50%)"	Steady-State	Steady-State	Vin Nominal	50%	*Alias Efficiency_Efficiency_nom
Steady-State	Steady-State	"SOURCE (INPUT-1, Nominal)"	"LOAD (OUTPUT-1, 60%)"	Steady-State	Steady-State	Vin Nominal	60%	*Alias Efficiency_Efficiency_nom
Steady-State	Steady-State	"SOURCE (INPUT-1, Nominal)"	"LOAD (OUTPUT-1, 70%)"	Steady-State	Steady-State	Vin Nominal	70%	*Alias Efficiency_Efficiency_nom
Steady-State	Steady-State	"SOURCE (INPUT-1, Nominal)"	"LOAD (OUTPUT-1, 80%)"	Steady-State	Steady-State	Vin Nominal	80%	*Alias Efficiency_Efficiency_nom
Steady-State	Steady-State	"SOURCE (INPUT-1, Nominal)"	"LOAD (OUTPUT-1, 90%)"	Steady-State	Steady-State	Vin Nominal	90%	*Alias Efficiency_Efficiency_nom
Steady-State	Steady-State	"SOURCE (INPUT-1, Nominal)"	"LOAD (OUTPUT-1, 100%)"	Steady-State	Steady-State	Vin Nominal	100%	*Alias Efficiency_Efficiency_nom
Steady-State	Steady-State	"SOURCE (INPUT-1, Maximum)"	"LOAD (OUTPUT-1, Light)"	Steady-State	Steady-State	Vin Maximum	Light Load	*Alias Efficiency_Efficiency_Max
Steady-State	Steady-State	"SOURCE (INPUT-1, Maximum)"	"LOAD (OUTPUT-1, 100%)"	Steady-State	Steady-State	Vin Maximum	100%	*Alias Efficiency_Efficiency_Max
Steady-State	Steady-State	"SOURCE (INPUT-1, Maximum)"	"LOAD (OUTPUT-1, 20%)"	Steady-State	Steady-State	Vin Maximum	20%	*Alias Efficiency_Efficiency_Max
Steady-State	Steady-State	"SOURCE (INPUT-1, Maximum)"	"LOAD (OUTPUT-1, 30%)"	Steady-State	Steady-State	Vin Maximum	30%	*Alias Efficiency_Efficiency_Max
Steady-State	Steady-State	"SOURCE (INPUT-1, Maximum)"	"LOAD (OUTPUT-1, 40%)"	Steady-State	Steady-State	Vin Maximum	40%	*Alias Efficiency_Efficiency_Max
Steady-State	Steady-State	"SOURCE (INPUT-1, Maximum)"	"LOAD (OUTPUT-1, 50%)"	Steady-State	Steady-State	Vin Maximum	50%	*Alias Efficiency_Efficiency_Max
Steady-State	Steady-State	"SOURCE (INPUT-1, Maximum)"	"LOAD (OUTPUT-1, 60%)"	Steady-State	Steady-State	Vin Maximum	60%	*Alias Efficiency_Efficiency_Max
Steady-State	Steady-State	"SOURCE (INPUT-1, Maximum)"	"LOAD (OUTPUT-1, 70%)"	Steady-State	Steady-State	Vin Maximum	70%	*Alias Efficiency_Efficiency_Max
Steady-State	Steady-State	"SOURCE (INPUT-1, Maximum)"	"LOAD (OUTPUT-1, 80%)"	Steady-State	Steady-State	Vin Maximum	80%	*Alias Efficiency_Efficiency_Max
Steady-State	Steady-State	"SOURCE (INPUT-1, Maximum)"	"LOAD (OUTPUT-1, 90%)"	Steady-State	Steady-State	Vin Maximum	90%	*Alias Efficiency_Efficiency_Max
Steady-State	Steady-State	"SOURCE (INPUT-1, Maximum)"	"LOAD (OUTPUT-1, 100%)"	Steady-State	Steady-State	Vin Maximum	100%	*Alias Efficiency_Efficiency_Max
Steady-State	Steady-State	"SOURCE (INPUT-1, Minimum)"	"LOAD (OUTPUT-1, Light)"	Steady-State	Steady-State	Vin Minimum	Light Load	*Alias Efficiency_Efficiency_Min
Steady-State	Steady-State	"SOURCE (INPUT-1, Minimum)"	"LOAD (OUTPUT-1, 100%)"	Steady-State	Steady-State	Vin Minimum	100%	*Alias Efficiency_Efficiency_Min
Steady-State	Steady-State	"SOURCE (INPUT-1, Minimum)"	"LOAD (OUTPUT-1, 20%)"	Steady-State	Steady-State	Vin Minimum	20%	*Alias Efficiency_Efficiency_Min
Steady-State	Steady-State	"SOURCE (INPUT-1, Minimum)"	"LOAD (OUTPUT-1, 30%)"	Steady-State	Steady-State	Vin Minimum	30%	*Alias Efficiency_Efficiency_Min
Steady-State	Steady-State	"SOURCE (INPUT-1, Minimum)"	"LOAD (OUTPUT-1, 40%)"	Steady-State	Steady-State	Vin Minimum	40%	*Alias Efficiency_Efficiency_Min
Steady-State	Steady-State	"SOURCE (INPUT-1, Minimum)"	"LOAD (OUTPUT-1, 50%)"	Steady-State	Steady-State	Vin Minimum	50%	*Alias Efficiency_Efficiency_Min
Steady-State	Steady-State	"SOURCE (INPUT-1, Minimum)"	"LOAD (OUTPUT-1, 60%)"	Steady-State	Steady-State	Vin Minimum	60%	*Alias Efficiency_Efficiency_Min
Steady-State	Steady-State	"SOURCE (INPUT-1, Minimum)"	"LOAD (OUTPUT-1, 70%)"	Steady-State	Steady-State	Vin Minimum	70%	*Alias Efficiency_Efficiency_Min
Steady-State	Steady-State	"SOURCE (INPUT-1, Minimum)"	"LOAD (OUTPUT-1, 80%)"	Steady-State	Steady-State	Vin Minimum	80%	*Alias Efficiency_Efficiency_Min
Steady-State	Steady-State	"SOURCE (INPUT-1, Minimum)"	"LOAD (OUTPUT-1, 90%)"	Steady-State	Steady-State	Vin Minimum	90%	*Alias Efficiency_Efficiency_Min
Steady-State	Steady-State	"SOURCE (INPUT-1, Minimum)"	"LOAD (OUTPUT-1, 100%)"	Steady-State	Steady-State	Vin Minimum	100%	*Alias Efficiency_Efficiency_Min

NoSimulation Steady-StateGenerate Efficiency Curves "CreateXYScalarPlot(AVG(LOAD) Efficiency_Min, AVG(LOAD) Efficiency_Min, DVM Vin Min, DVM Efficiency, Al, vert, xlabel=Load Current xunit=sk ylabel=Efficiency units=xxx showpoint=true color=green)"
"CreateXYScalarPlot(AVG(LOAD) Efficiency_Max, AVG(LOAD) Efficiency_Max, DVM Vin Max, DVM Efficiency, Al, vert, xlabel=Load Current xunit=sk ylabel=Efficiency units=xxx showpoint=true color=red)"
"CreateXYScalarPlot(AVG(LOAD) Efficiency_Max, AVG(LOAD) Efficiency_Max, DVM Vin Max, DVM Efficiency, Al, vert, xlabel=Load Current xunit=sk ylabel=Efficiency units=xxx showpoint=true color=blue)"

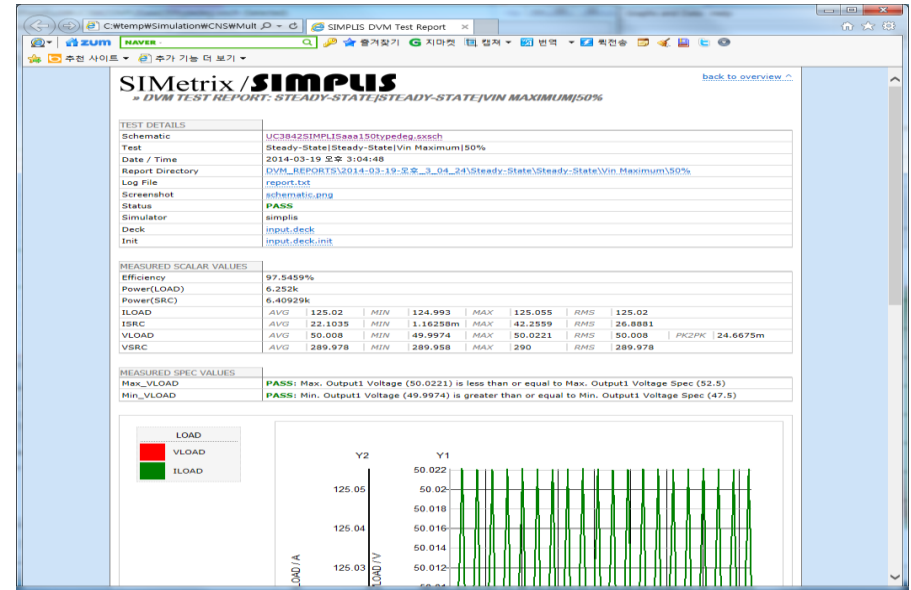

DC/DC Converter Efficiency Test Plan

Test Report