

SIMPLIS/SIMetrix

전원 CM 노이즈 평가 응용

Samsung Electronics, Ltd.

JeongGyu.Park

Contents

- **About Common mode noise..**

- . What's the C.M noise among many coupling routes
- . Why we need to consider C.M noise

- **Power System level analysis**

- . Which factor can effect on C.M noise issue (parasitic L, C, etc..)
- . Obtain clear signal measurement by changing C.M current return path
- . Common mode Voltage ripple & noise Current decrease by changing Y-cap


- **Simulation for C.M noise**

- . Circuits side
- . Minimize the power GND return current path
- . Minimize the C.M current return path


[EMI] Noise coupling route

- 4 standard kinds of noise coupling


Conductive

 


Inductive

 


Capacitive

 

Radiated;
Antenna Effect


 


PCB E-field, H-field

 


*출처 : EMC papers


Noise Coupling in PDN

  


• What is Common mode noise?

 

*Radiation to cable

 


*PCB Capacitive coupling

 


*출처 : EMC papers

 Digital weakly specified I2C signal vs. Noisy Power line cable



Signal &
Power cable

 


Server or PC
system


● I2C line voltage noise under interfering with Power lines

. Noises are **Synch.** to the switching frequency of Power





Faster Switch or some coupling line

 

Slow Switch

 


    - RE EMI source → Differential and Common mode noise (Primary +Vin ~ GND)
 . FET Vds ringing noise level : 25V(Fast Switch) > 20V(Slow Switch) : **5[dB] scale margin**








. RE noise

 - Single b'd : only → 6.7V peak to peak(same /w simulation) vs. Multi b'd




B'd 'A', B'd 'B' : Y-cap line 보드내 연결 전/후

     ※ B'd 'B'에 FET Rising Switching이 빠른 것(Typ. 4nS) 으로 적용 후 측정 data




CM Ground voltage Gap (Relative CM leakage value)


- Load & PCB return-L effect

 


1nH, 5nF
85W/base
B'd 'A' case

 


1nH, 5nF
260W $\uparrow$
B'd 'B' case

 


2nH $\uparrow$, 5nF
85W

 

1nH, 5nF
85W, Slow
FET(20nS Tr.)

 


Vin GND
~ PCB DGND
 $\rightarrow$ Stable

 


CM 1st~2nd Ground voltage gap Simulation

- Add B'd 'B' x1pcs on the back

 


1nH,5nF
85W/base

 


Design guide #1

 1nH,5nF
B'd 'A' + B'd 'B'
*Vin+ Y-cap added




1nH,5nF
B'd 'A' + B'd 'B'

 


CM 1st~2nd Ground voltage gap Simulation

- Add x3 b'd on the back

 

Parameter sweep(Multi-step)

 


Multi-Sweep result (~x 3 running time)




[C.M Current return path]


Intensify the noise sink path

 

[Appendix 1] Common Mode current Path

 


[Appendix 2.1] Common Mode current Path

 

[Appendix 2.2] Common Mode Y-cap


- With Base plate, effective Y-cap position
- "Y" capacitors are added to provide a lower impedance path for current to flow and to reduce the level of common mode voltage that appears between L-N and ground.(Fr. Application note)

 


[Appendix 2.3] Common Mode Y-cap effect

- With Base plate, effective Y-cap

→ With 4700pF capacitor added on C3, CM voltage dropped to 700mV p/p from 4V p/p.

 

[Appendix 3] /w Other tools

 

- F.Bridge control

/w C.M parameter change
→ Gain similar Results

